

Exo 1

① $C = A \times \Delta$

② $I = \frac{\delta Q}{dt} = \frac{qnSv dt}{dt} = qnSv \stackrel{q=-e}{\downarrow} = -enSv$


AN $I = -1,6 \cdot 10^{-19} \times 2 \cdot 10^{29} \times 1 \times 10^{-6} \times 50 \cdot 10^{-6}$
 $= -1,6 \times \underbrace{100}_{10^2} \times \underbrace{10^{-13+29-6-6}}_{10^{-2}}$
 $= -1,6 \text{ A}$

Exo 2


① Par application du pont diviseur de tension, on a $\begin{cases} u_1 = \frac{R_1}{R_1+R_2} u \\ u_2 = -\frac{R_2}{R_1+R_2} u \end{cases}$

② $u_1 = \frac{u}{2} \Leftrightarrow R_1 = R_2$


Exo 3.

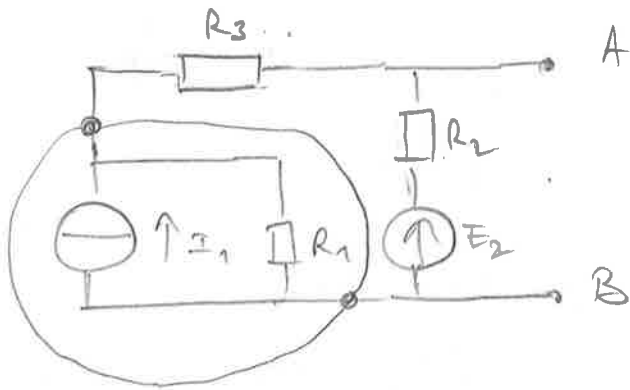


Th./Nort

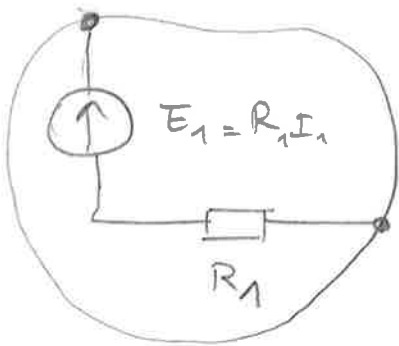

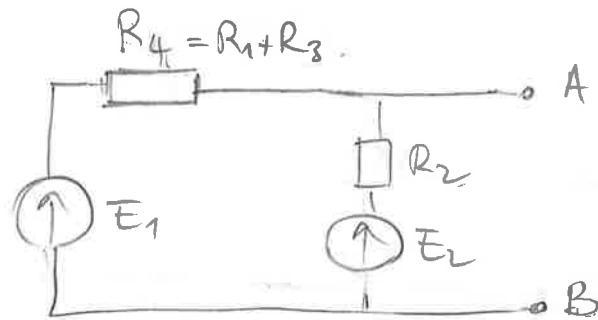
Alors R_2 et R_3 se retrouvent en série. Ainsi :




Th./Nort

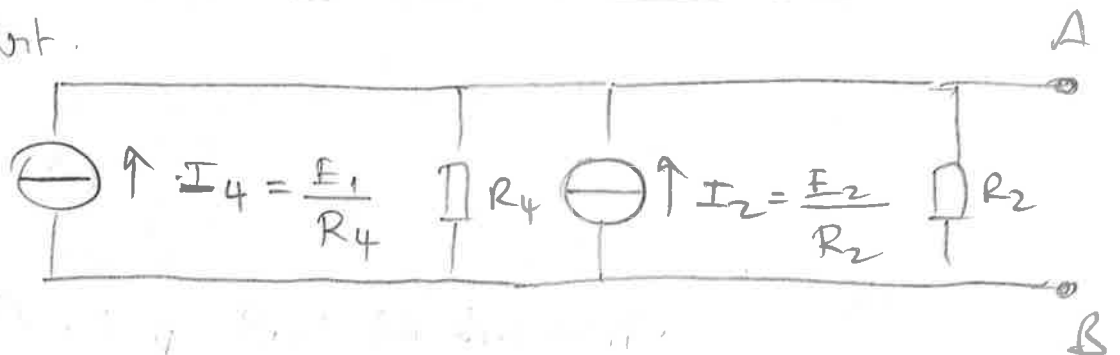

Associe //

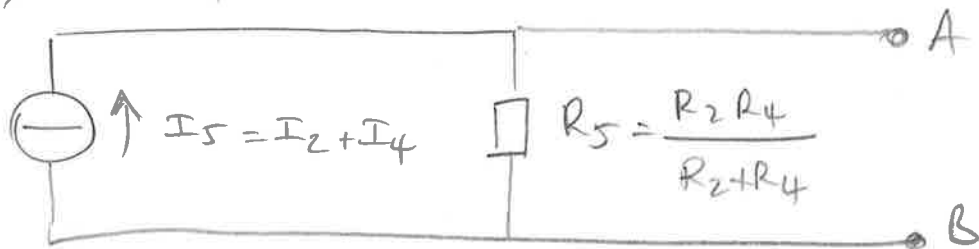

Th./Nort

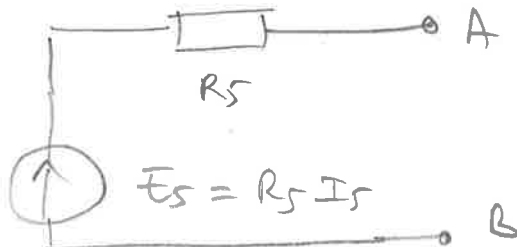

Exo 4

① $u = V_A - V_B$.

② $i_1 = -\frac{u}{R_1}$

$$i_2 = \frac{u}{2R_2}$$

$$u = E - Ri \Leftrightarrow i = \frac{E - u}{R}$$

$$i = i_2 - i_1$$

$$\Rightarrow \frac{E - u}{R} = \frac{u}{2R_2} + \frac{u}{R_1}$$


$$\Leftrightarrow u \times \left(\frac{1}{2R_2} + \frac{1}{R_1} + \frac{1}{R} \right) = \frac{E}{R}$$

On pose R_{eq} tel que $\frac{1}{2R_2} + \frac{1}{R_1} = \frac{1}{R_{eq}}$.

$$\text{Alors } u \times \left(\frac{1}{R_{eq}} + \frac{1}{R} \right) = \frac{E}{R}$$

$$\Leftrightarrow u = \frac{E/R}{\frac{1}{R_{eq}} + \frac{1}{R}} = \frac{R_{eq}}{R + R_{eq}} \times E$$

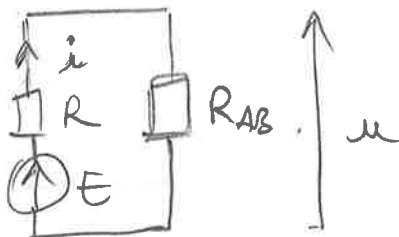③ R_2 et R_2 en série
 R_1 en // avec $R_2 + R_2$) $\Rightarrow R_{AB} = \frac{2R_2 \times R_1}{R_1 + 2R_2} = R_{eq}$.



$$i = \frac{E}{R + R_{AB}}$$

$$u = R_{AB} \times i = \frac{R_{AB}}{R + R_{AB}} \times E$$

\Rightarrow exprimez quelque $R_{AB} = R_{eq}$.

